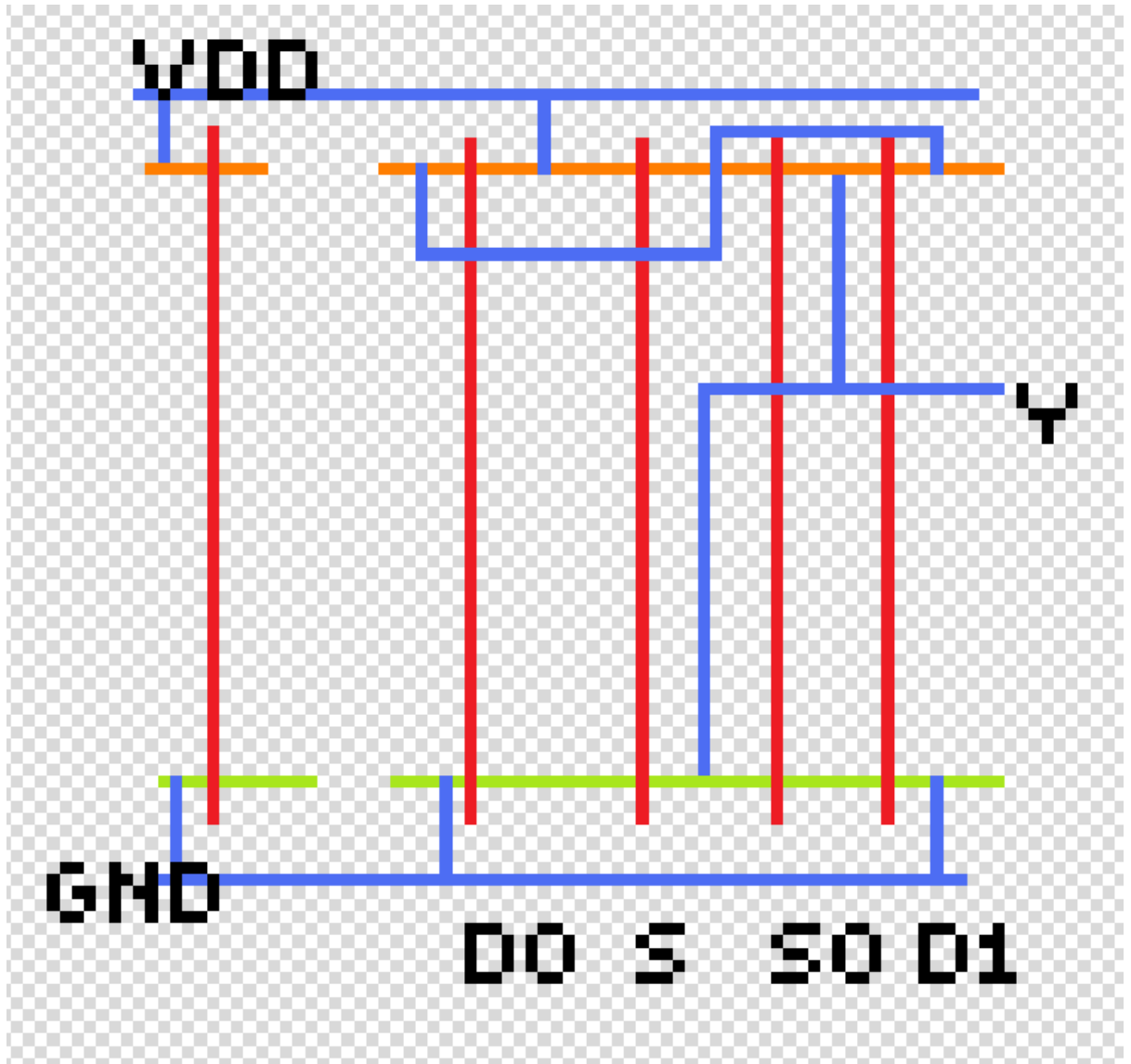


Gebze Technical University
Computer Engineering Department


CSE 436 Digital Integrated Circuit
Homework #3

Berkan AKIN
171044073


❖ Below is the 2x1 stick diagram design.



❖ Below is the 2x1 mux magic design.

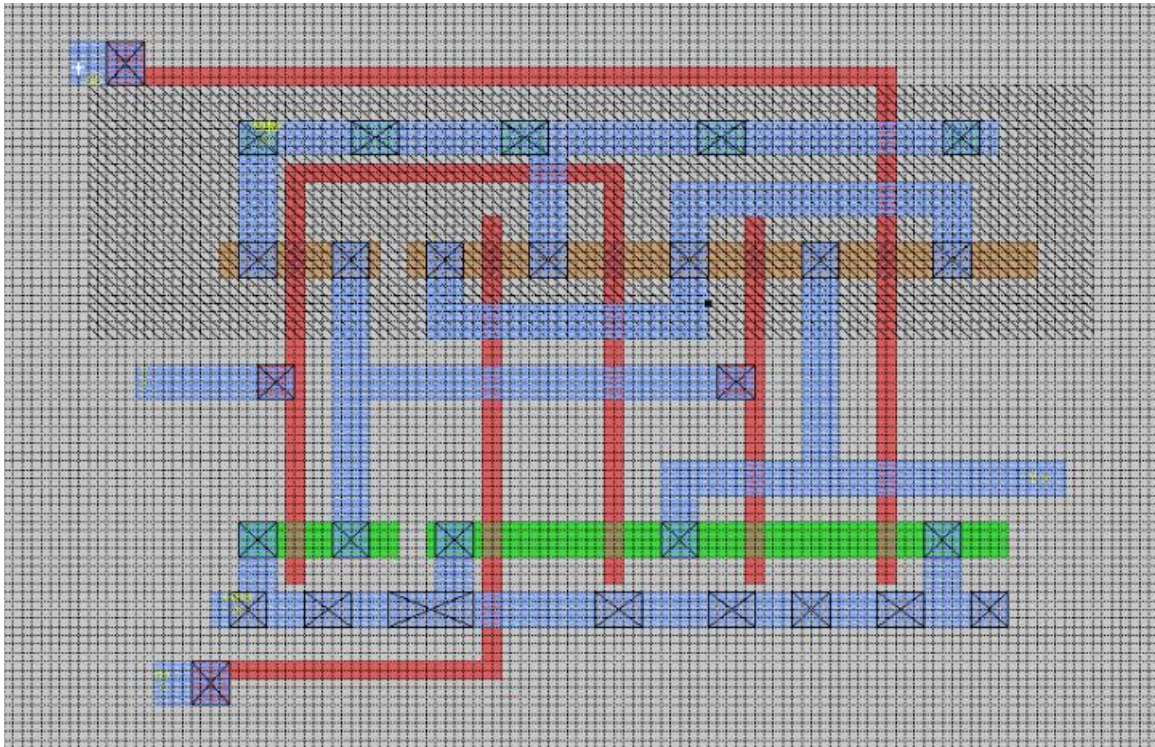

❖ Below is the 4x1 mux magic design.

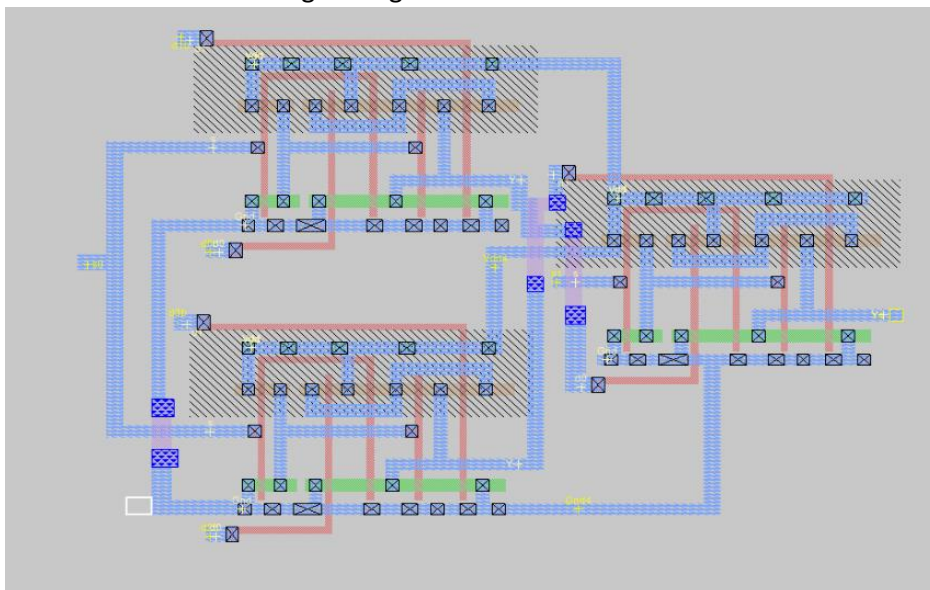


2x1 Mux Text Case

S = orange Y = Green

D0 = red D1 = Blue

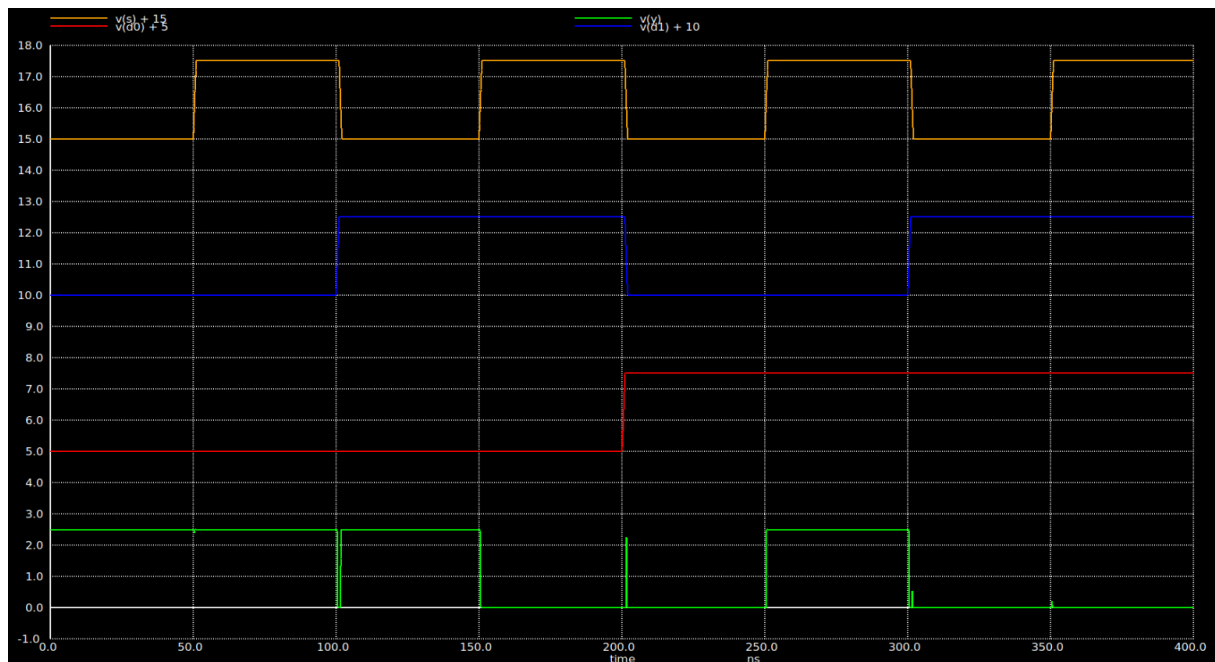All expected results for the 2x1 multiplexer have turned out correctly.




Spice File

```
57 VDD Vdd 0 2.5
58
59 VD0 d0 0 PULSE(0 2.5V 200ns 0 0 200ns 400ns)
60 VD1 d1 0 PULSE(0 2.5V 100ns 0 0 100ns 200ns)
61 VS s 0 0 PULSE(0 2.5V 50ns 0 0 50ns 100ns)
62
63
64 .OPTIONS TEMP=25 reltol=1e-6
65 .tran 1NS 400NS
66
67 .control
68 run
69
70 plot V(d0) + 5 V(d1) + 10 V(s) + 15 V(Y)
71
72 .endc
73 .end
```

- ❖ There was an error in the combination for the 4x1 multiplexer; **the expected results couldn't be obtained**. Below are the combined forms of the 2x1 multiplexers and the test results.

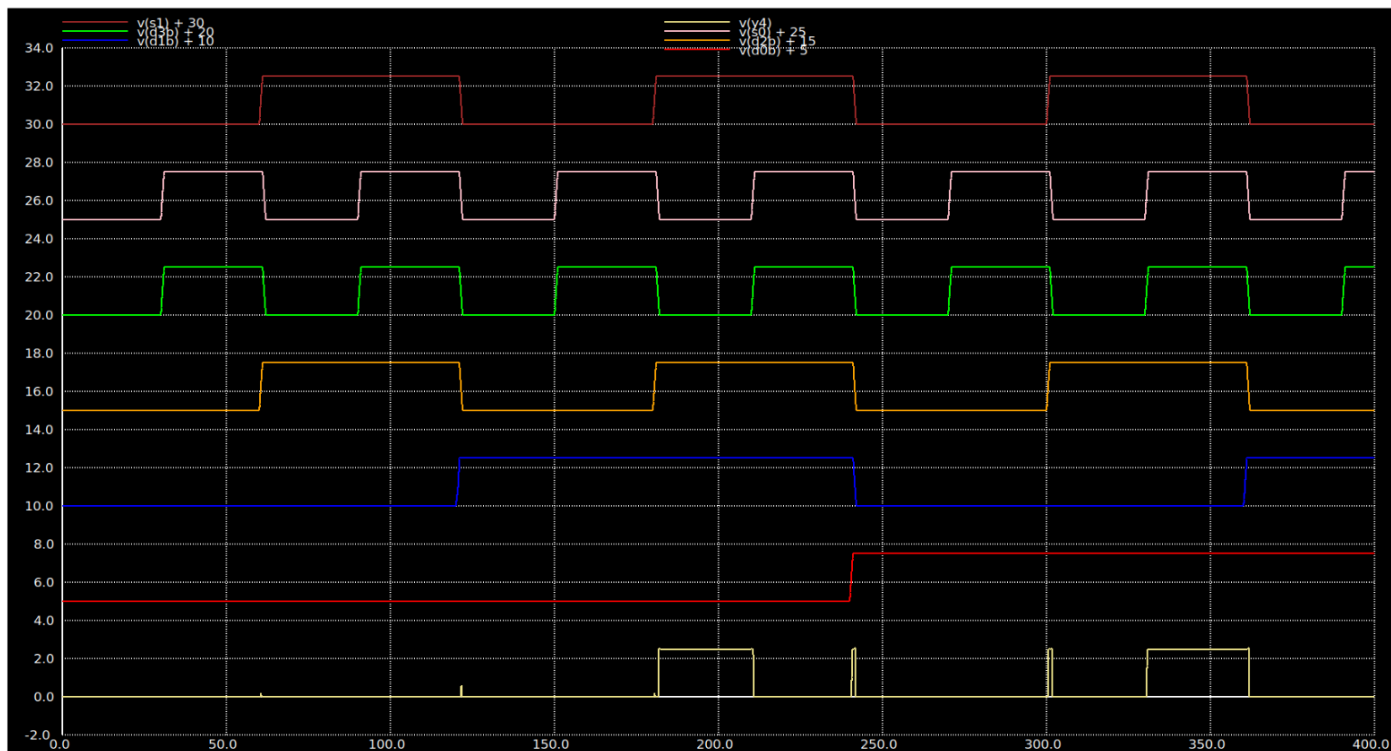S1 = Dark Red S0 = purple d3b = green d2b = orange d1 = blue d0 = red y = yellow



Spice File

```

144
145 VDD Vdd4 0 2.5
146
147 VGND Gnd4 0 0
148
149 VD0 d0b 0 PULSE(0 2.5V 240ns 0 0 240ns 480ns)
150 VD1 d1b 0 PULSE(0 2.5V 120ns 0 0 120ns 240ns)
151 VD2 d2b 0 PULSE(0 2.5V 60ns 0 0 60ns 120ns)
152 VD3 d3b 0 PULSE(0 2.5V 30ns 0 0 30ns 60ns)
153 VS1 s1 0 0 PULSE(0 2.5V 60ns 0 0 60ns 120ns)
154 VS0 s0 0 0 PULSE(0 2.5V 30ns 0 0 30ns 60ns)
155
156
157 .OPTIONS TEMP=25 reltol=1e-6
158 .tran 1NS 400NS
159
160 .control
161 run
162
163 plot V(d0b) + 5 V(d1b) + 10 V(d2b) + 15 V(d3b) + 20 V(s0) + 25 V(s1) + 30 V(Y4)
164
165 .endc
166 .end

```