


**Gebze Technical University**  
**Computer Engineering Department**

**CSE 436 Digital Integrated Circuit**  
**Homework #1**


**Berkan AKIN**  
**171044073**

- In accordance with the request, two designs have been created. First, a design with  $4\lambda/2\lambda$  NMOS and PMOS transistors was made, and then an  $8\lambda/2\lambda$  PMOS transistor was designed. The two different inverters that have been designed are shown below..

#### $4\lambda/2\lambda$ NMOS and PMOS

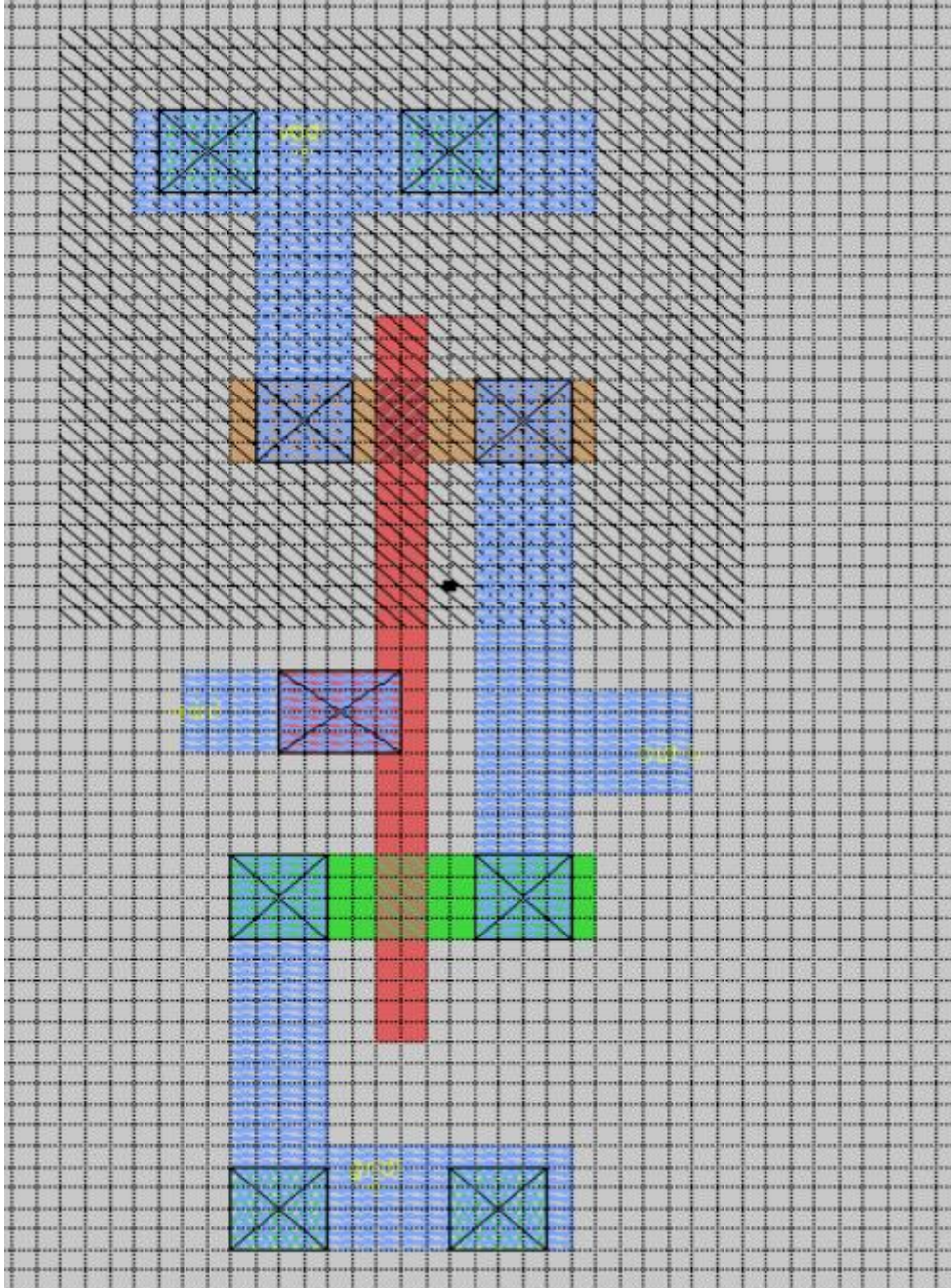

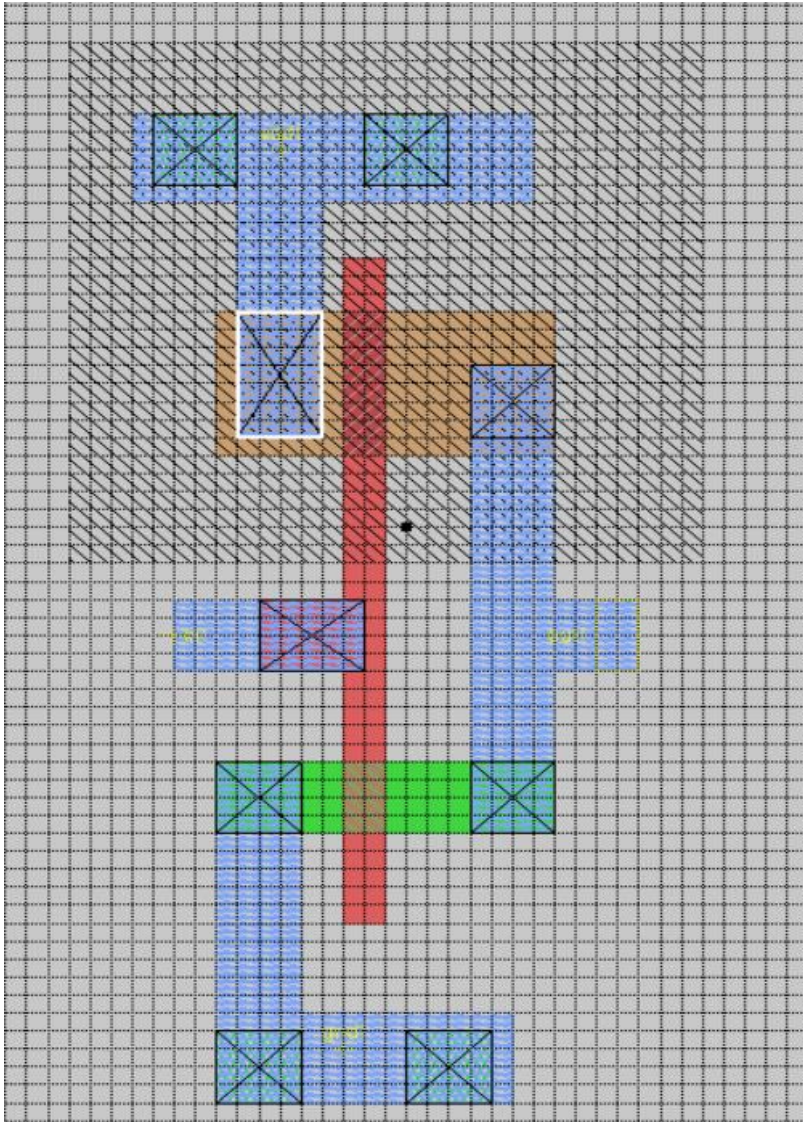
$4\lambda/2\lambda$  NMOS and  $8\lambda/2\lambda$  PMOS






- Two different transistors have been tested with NG Spice, and the test results are presented below.


#### $4\lambda/2\lambda$ NMOS and PMOS

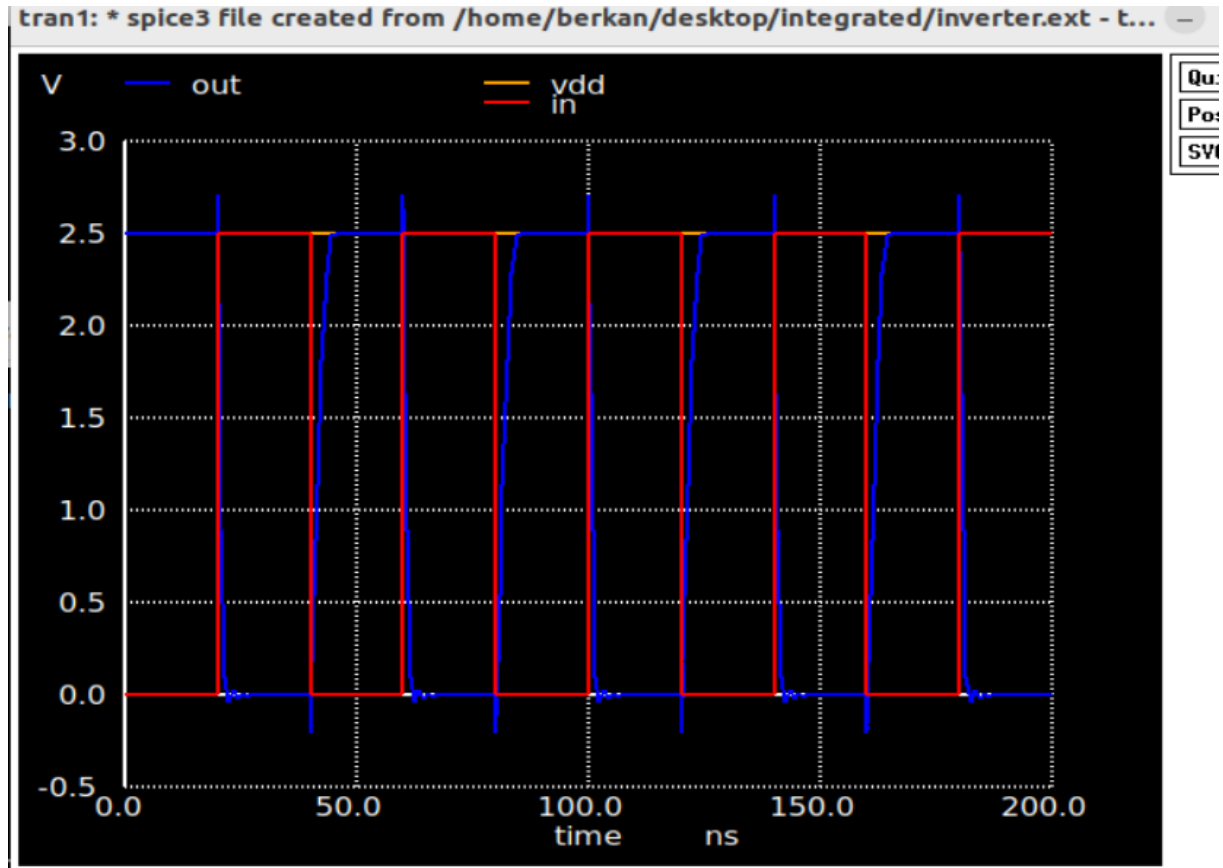
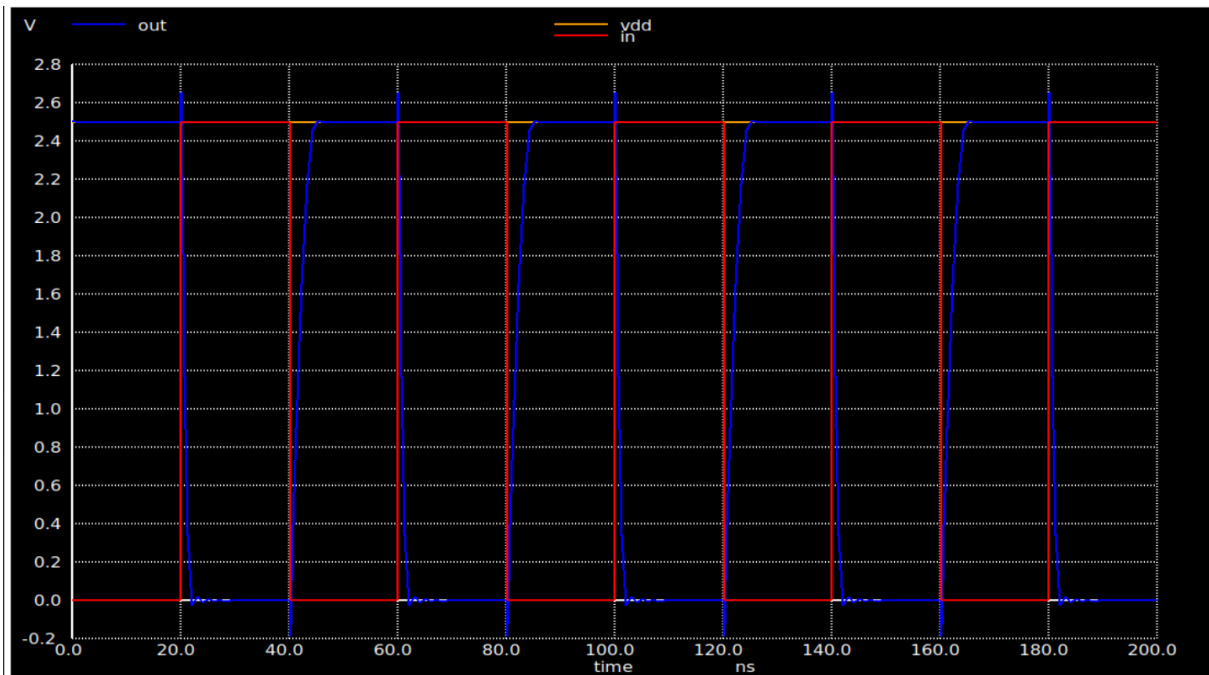
## $4\lambda/2\lambda$ NMOS and $8\lambda/2\lambda$ PMOS



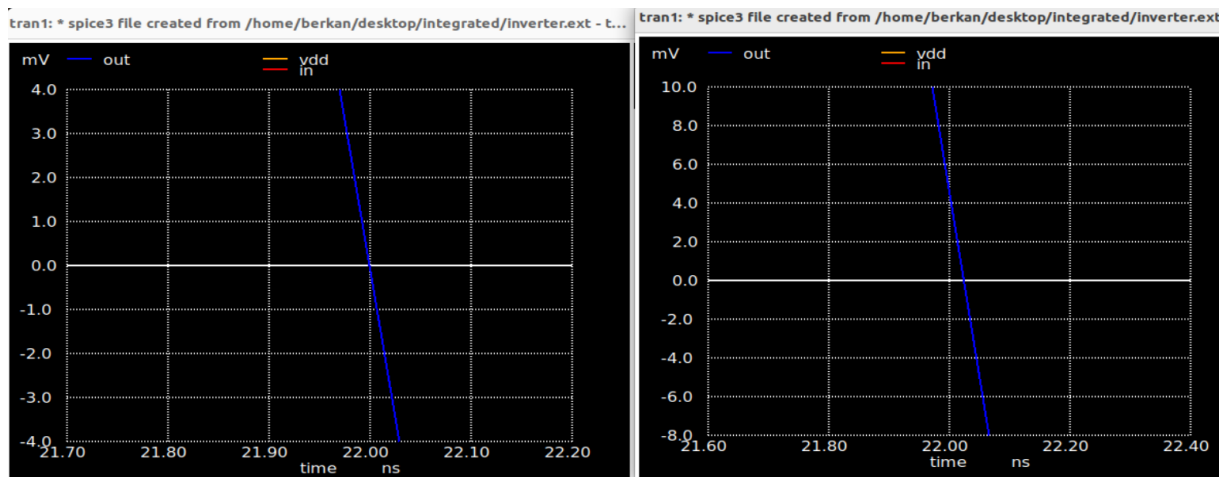- When the response times of the two inverters are compared, it is observed that the inverter made with the  $8\lambda/2\lambda$  PMOS transistor has a delay. The delay can be seen in the comparative image below. The inverter on the right has an  $8\lambda/2\lambda$  PMOS, while the one on the left has a  $4\lambda/2\lambda$  PMOS



- The delay on the left with the  $4\lambda/2\lambda$  is less, while on the right with the  $8\lambda/2\lambda$ , the delay is more apparent.

